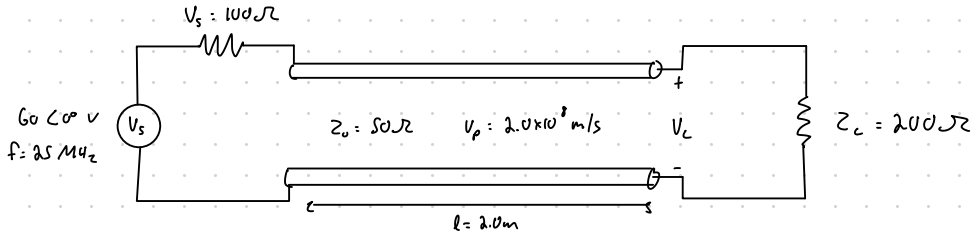


Exercise: for the lossless transmission line presented in figure 1.1, find the load voltage V_L . Write a MATLAB program to plot the load voltage V_L v.s. time. Is the magnitude of the load voltage V_L a function of the source frequency f ? If it is, plot $|V_L|$ v.s. f ; if not, explain.



At any point on the line the voltage is given by:

$$V_s(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} = V_0^+ (e^{-\gamma z} + \Gamma_L e^{+\gamma z})$$

@ the load, $z = 0$. Therefore:

$$V_L = V_0^+ (1 + \Gamma_L)$$

Then we need to find V_0^+ and Γ_L . We have:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{200 - 50}{200 + 50} = \frac{150}{250} = \frac{3}{5} = 0.6$$

Finding V_0^+ requires we know the input impedance Z_{in} . For a lossless transmission line:

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)} = (50) \frac{200 + j 50 \tan(\beta l)}{50 + j 200 \tan(\beta l)}$$

$\beta = \frac{\omega}{v_p} = \frac{2\pi f}{v_p} = \frac{2\pi (2.5 \times 10^6)}{2 \times 10^8}$
 $\beta = \frac{\pi}{4} \text{ rad/m}, l = 2$
 $\beta l = \frac{\pi}{2}$

$$Z_{in} = 12.5 \Omega$$

Then we can calculate the input voltage V_{in} :

$$V_{in} = V_s \frac{Z_{in}}{Z_s + Z_{in}} = 60 \cdot \frac{12.5}{100 + 12.5} = 6.67 \angle 0^\circ \text{ V}$$

Now we have for the forward voltage:

$$V_0^+ = \frac{V_{in}}{e^{+\gamma l} + \Gamma_L e^{-\gamma l}} ; \gamma l = (\alpha + j\beta)l = j\beta l$$

$\alpha = 0$ since line is lossless
 $\beta l = \frac{\pi}{2}$

$$= \frac{6.67}{e^{j\frac{\pi}{2}} + 0.6 e^{-j\frac{\pi}{2}}} = \frac{6.67}{-j + 0.6j} = \frac{6.67}{-0.4j} = -16.675j = 16.675 e^{-j\frac{\pi}{2}} \text{ V}$$

Finally:

$$V_L = V_0^+ (1 + \Gamma_L) = 16.675 e^{-j\frac{\pi}{2}} (1 + 0.6) = 26.675 e^{-j\frac{\pi}{2}} \text{ V}$$

Convert this phasor into its instantaneous form gives us the voltage across the load:

$$V_L = |V_L| \cos(\omega t + \angle V_L) \quad ; \quad \omega = 2\pi f = 2\pi (25 \times 10^6) \approx 1.57 \times 10^8 \text{ rad/s}$$

$$V_L = 26.675 \cos(1.57 \times 10^8 t - \frac{\pi}{2})$$

Is the magnitude of the load voltage V_L a function of the source frequency f ?

Yes, $|V_L|$ is a function of the source frequency f .

This is because Z_{in} and the factors $e^{\pm j\beta l}$ depend on $\beta = \frac{2\pi f}{v_p}$. Only at the given frequency $f = 25 \text{ MHz}$ does the line behave as a quarter-wave transformer with $Z_{in} = Z_0^*/Z_L$. Away from this frequency, both the magnitude and phase of V_L vary with f .

In the example we saw for this set, the $|V_L|$ was not a function of f because both the input Z_{in} and the source resistance Z_s are real, and the magnitude of V_{in} doesn't vary as f varies. The difference between this example and our exercise is in the example: $Z_L = Z_0 \Rightarrow \Gamma_L = 0$. This results in no reflections, no standing waves, and the line looking like a single resistor Z_0 at all frequencies $\Rightarrow |V_L|$ is independent of f .